

# Digital Logic & Computer Design CS 4341

Professor Dan Moldovan  
Spring 2010

Copyright © 2007 Elsevier

7-<1>



## Chapter 7 :: Microarchitecture

*Digital Design and Computer Architecture*

David Money Harris and Sarah L. Harris

Copyright © 2007 Elsevier

7-<2>



## Chapter 7 :: Topics

- Introduction
- Performance Analysis
- Single-Cycle Processor
- Multicycle Processor
- Pipelined Processor
- Exceptions
- Advanced Microarchitecture

Copyright © 2007 Elsevier

7-<3>



## Introduction

- Microarchitecture: how to implement an architecture in hardware
- Processor:
  - Datapath: functional blocks
  - Control: control signals

Application Software	programs
Operating Systems	device drivers
Architecture	instructions registers
Micro-architecture	datapaths controllers
Logic	adders memories
Digital Circuits	AND gates NOT gates
Analog Circuits	amplifiers filters
Devices	transistors diodes
Physics	electrons

Copyright © 2007 Elsevier

7-<4>



## Microarchitecture

- Multiple implementations for a single architecture:
  - Single-cycle
    - Each instruction executes in a single cycle
  - Multicycle
    - Each instruction is broken up into a series of shorter steps
  - Pipelined
    - Each instruction is broken up into a series of steps
    - Multiple instructions execute at once.

Copyright © 2007 Elsevier

7-<5>



## Processor Performance

- Program execution time
  - Execution Time = (# instructions)(cycles/instruction)(seconds/cycle)**
- Definitions:
  - Cycles/instruction = CPI
  - Seconds/cycle = clock period
  - $1/\text{CPI} = \text{Instructions/cycle} = \text{IPC}$
- Challenge is to satisfy constraints of:
  - Cost
  - Power
  - Performance

Copyright © 2007 Elsevier

7-<6>



## MIPS Processor

- We consider a subset of MIPS instructions:
  - R-type instructions: and, or, add, sub, slt
  - Memory instructions: lw, sw
  - Branch instructions: beq
- Later consider adding addi and j

Copyright © 2007 Elsevier

7-<7>



## Architectural State


- Determines everything about a processor:
  - PC
  - 32 registers
  - Memory

Copyright © 2007 Elsevier

7-<8>



## MIPS State Elements

 

Copyright © 2007 Elsevier

7-<9>



## Single-Cycle MIPS Processor

- Datapath
- Control


Copyright © 2007 Elsevier

7-<10>


 
## Single-Cycle Datapath: lw fetch

- First consider executing lw
- **STEP 1:** Fetch instruction




Copyright © 2007 Elsevier

7-<11>


 
## Single-Cycle Datapath: lw register read

- **STEP 2:** Read source operands from register file




Copyright © 2007 Elsevier

7-<12>



## Single-Cycle Datapath: lw immediate

- **STEP 3:** Sign-extend the immediate

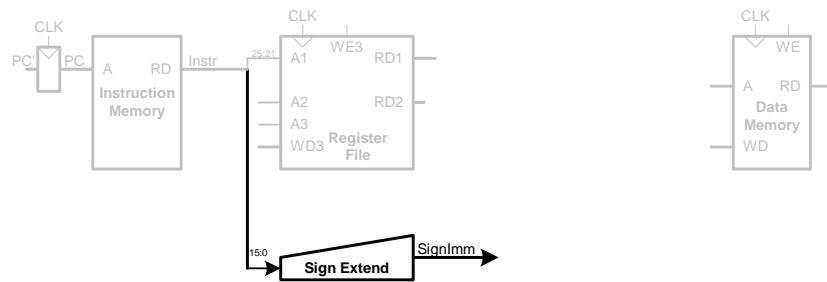


Copyright © 2007 Elsevier

7-<13>



## Single-Cycle Datapath: lw address

- **STEP 4:** Compute the memory address

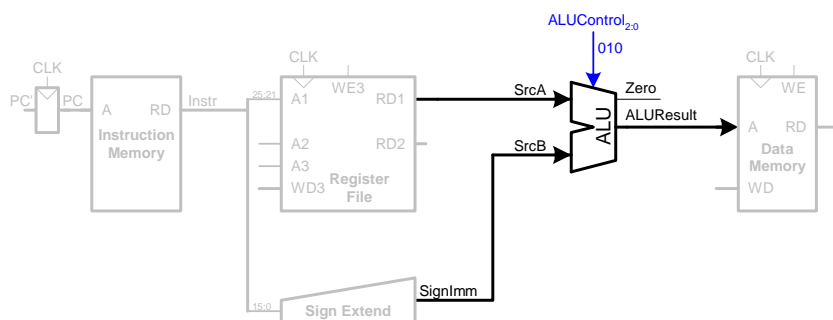


Copyright © 2007 Elsevier

7-<14>


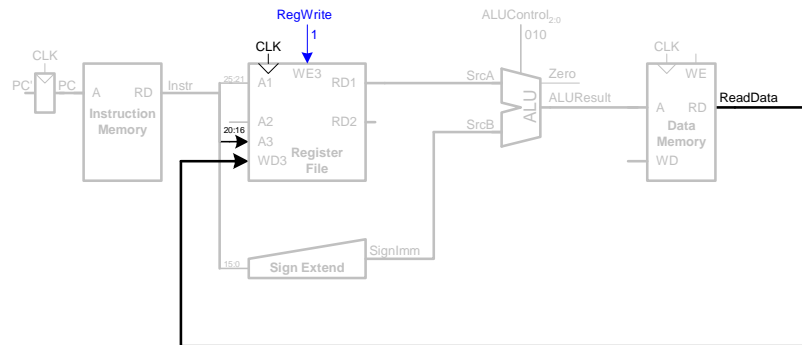
## Single-Cycle Datapath: 1W memory read

- **STEP 5:** Read data from memory and write it back to register file




Copyright © 2007 Elsevier

7-<15>


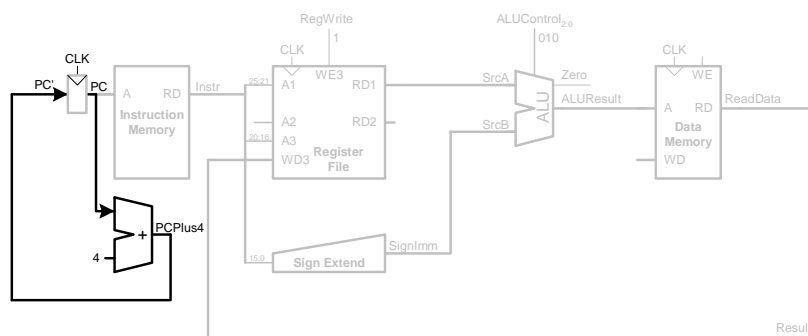
## Single-Cycle Datapath: 1W PC increment

- **STEP 6:** Determine the address of the next instruction



Copyright © 2007 Elsevier


7-<16>





## Single-Cycle Datapath: SW

- Write data in  $rt$  to memory

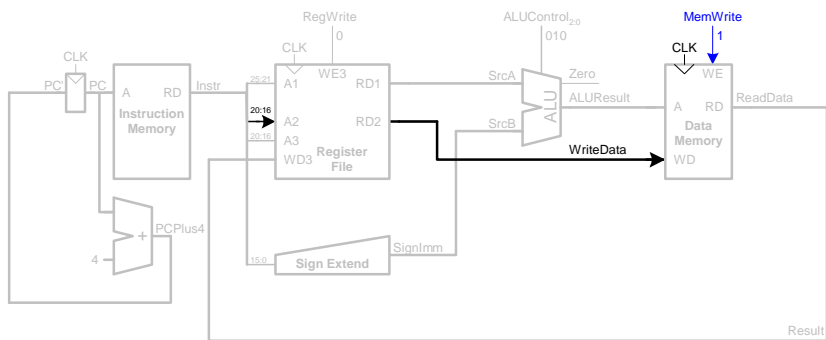


Copyright © 2007 Elsevier

7-<17>


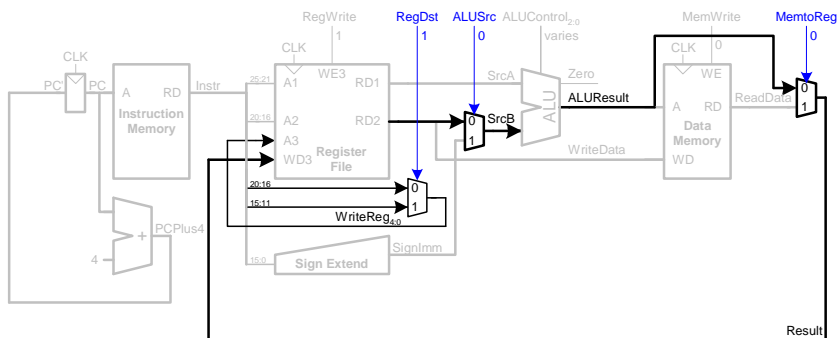
## Single-Cycle Datapath: R-type instructions

- Read from  $rs$  and  $rt$
- Write  $ALUResult$  to register file
- Write to  $rd$  (instead of  $rt$ )



Copyright © 2007 Elsevier


7-<18>


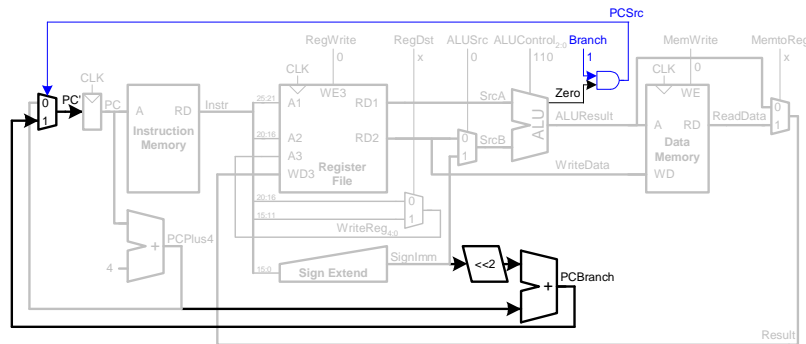
## Single-Cycle Datapath: beq

- Determine whether values in `rs` and `rt` are equal
- Calculate branch target address:  

$$\text{BTA} = (\text{sign-extended immediate} \ll 2) + (\text{PC}+4)$$




Copyright © 2007 Elsevier

7-<19>



## Complete Single-Cycle Processor

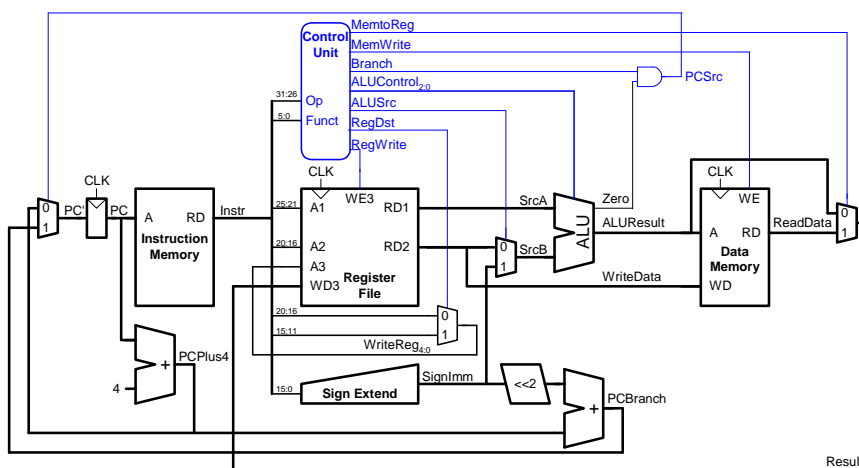


Copyright © 2007 Elsevier

7-<20>



## Control Unit

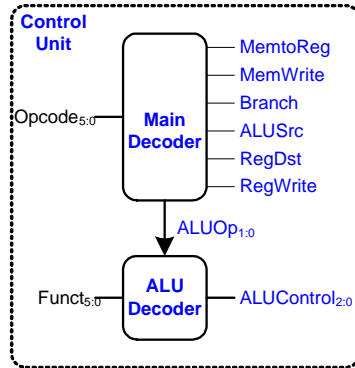


Copyright © 2007 Elsevier

7-<21>



## Review: ALU

 


F <sub>2:0</sub>	Function
000	A & B
001	A   B
010	A + B
011	not used
100	A & ~B
101	A   ~B
110	A - B
111	SLT

Copyright © 2007 Elsevier

7-<22>



## Review: ALU

 

Copyright © 2007 Elsevier

7-<23>



## Control Unit: ALU Decoder

$ALUOp_{1:0}$	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

$ALUOp_{1:0}$	Funct	$ALUControl_{2:0}$
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)


Copyright © 2007 Elsevier

7-<24>



## Control Unit: Main Decoder

Instruction	Op <sub>5:0</sub>	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemoReg	ALUOp <sub>1:0</sub>
R-type	000000							
lw	100011							
sw	101011							
beq	000100							

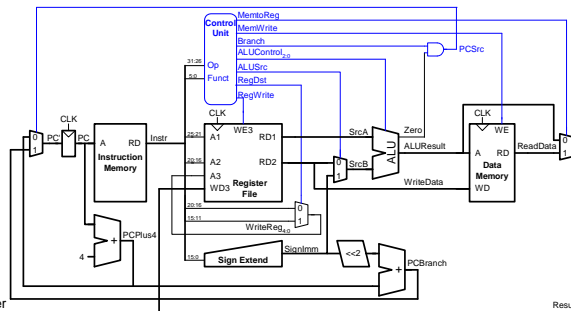

Copyright © 2007 Elsevier

7-<25>



## Control Unit: Main Decoder


Instruction	Op <sub>5:0</sub>	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemoReg	ALUOp <sub>1:0</sub>
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

Copyright © 2007 Elsevier

7-<26>



## Single-Cycle Datapath Example: or

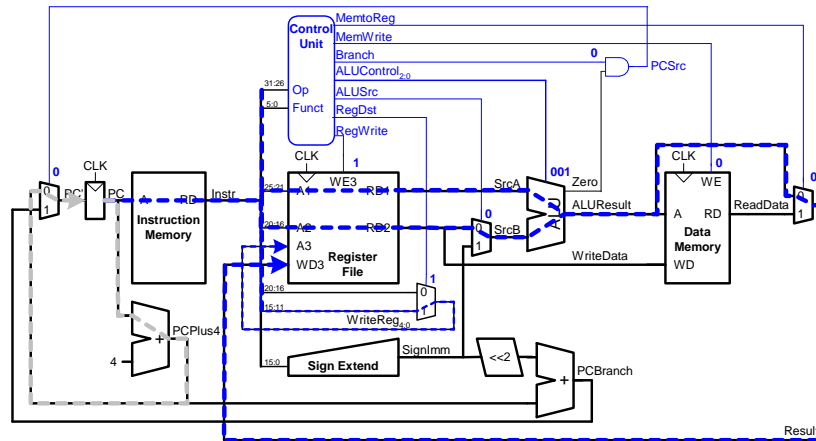


Copyright © 2007 Elsevier

7-<27>



## Extended Functionality: addi

- No change to datapath

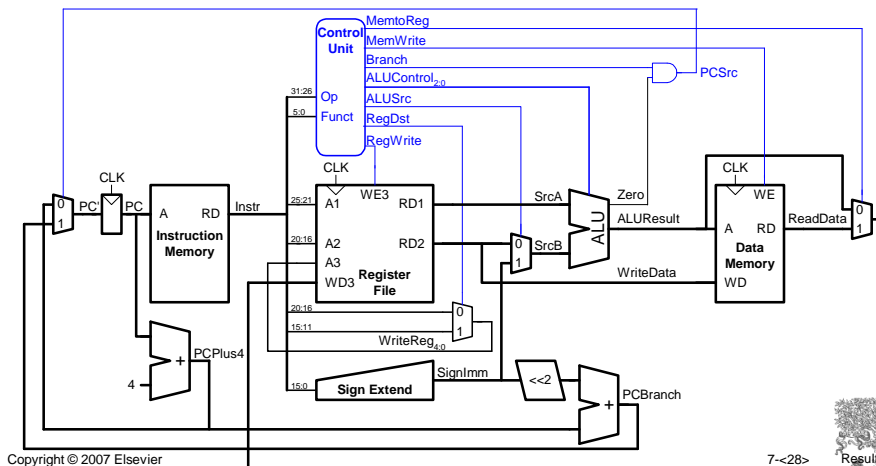

Copyright © 2007 Elsevier

7-<28>



## Control Unit: addi

Instruction	Op <sub>5:0</sub>	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemoReg	ALUOp <sub>1:0</sub>
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
<b>addi</b>	<b>001000</b>							

Copyright © 2007 Elsevier

7-<29>



## Control Unit: addi


Instruction	Op <sub>5:0</sub>	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemoReg	ALUOp <sub>1:0</sub>
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
<b>addi</b>	<b>001000</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>00</b>

Copyright © 2007 Elsevier

7-<30>



## Extended Functionality: j

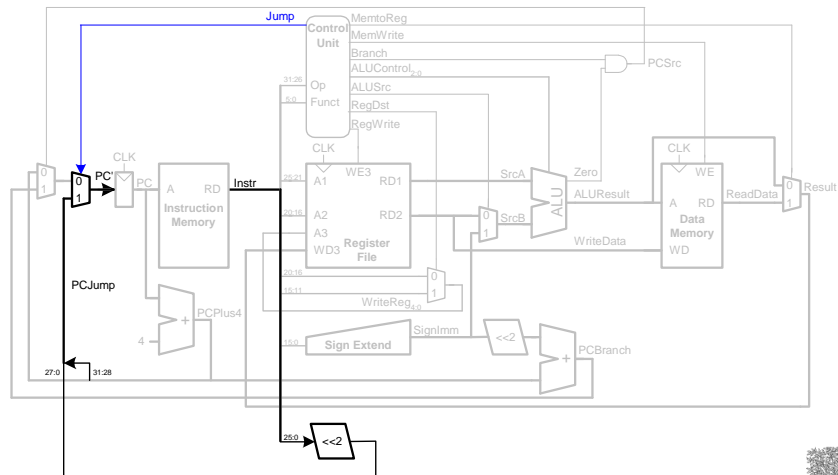

Copyright © 2007 Elsevier

7-<31>



## Control Unit: Main Decoder

Instruction	Op <sub>5:0</sub>	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp <sub>1:0</sub>	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
<b>j</b>	<b>000100</b>								

Copyright © 2007 Elsevier

7-<32>





## Control Unit: Main Decoder

Instruction	Op <sub>5:0</sub>	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp <sub>1:0</sub>	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	<b>000100</b>	<b>0</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>0</b>	<b>X</b>	<b>XX</b>	<b>1</b>

Copyright © 2007 Elsevier

7-<33>



## Review: Processor Performance

### Program Execution Time

$$= (\# \text{ instructions})(\text{cycles/instruction})(\text{seconds/cycle})$$

$$= \# \text{ instructions} \times \text{CPI} \times T_C$$


Copyright © 2007 Elsevier

7-<34>


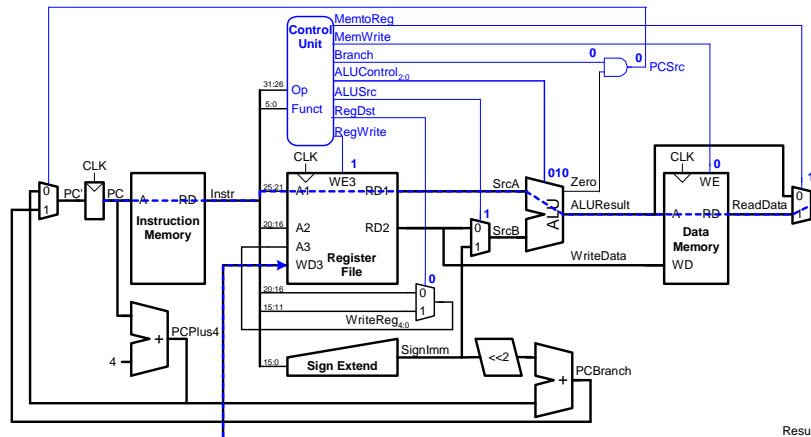
## Single-Cycle Performance

- $T_c$  is limited by the critical path (1w)



Copyright © 2007 Elsevier

7-<35>



## Single-Cycle Performance

- Single-cycle critical path:

$$T_c = t_{pcq\_PC} + t_{mem} + \max(t_{RFread}, t_{sext} + t_{mux}) + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- In most implementations, limiting paths are:

- memory, ALU, register file.
- $T_c = t_{pcq\_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup}$

Copyright © 2007 Elsevier

7-<36>



## Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$T_c =$

Copyright © 2007 Elsevier

7-<37>



## Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}
 T_c &= t_{pcq\_PC} + 2t_{mem} + t_{RFread} + t_{mux} + t_{ALU} + t_{RFsetup} \\
 &= [30 + 2(250) + 150 + 25 + 200 + 20] \text{ ps} \\
 &= 925 \text{ ps}
 \end{aligned}$$

Copyright © 2007 Elsevier

7-<38>



## Single-Cycle Performance Example

- For a program with 100 billion instructions executing on a single-cycle MIPS processor,

Execution Time =

Copyright © 2007 Elsevier

7-<39>



## Single-Cycle Performance Example

- For a program with 100 billion instructions executing on a single-cycle MIPS processor,

$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_C \\ &= (100 \times 10^9)(1)(925 \times 10^{-12} \text{ s}) \\ &= 92.5 \text{ seconds}\end{aligned}$$

Copyright © 2007 Elsevier

7-<40>



## Multicycle MIPS Processor

- Single-cycle microarchitecture:
  - + simple
  - cycle time limited by longest instruction (1w)
  - two adders/ALUs and two memories
- Multicycle microarchitecture:
  - + higher clock speed
  - + simpler instructions run faster
  - + reuse expensive hardware on multiple cycles
  - sequencing overhead paid many times
- Same design steps: datapath & control


Copyright © 2007 Elsevier

7-<41>


 
## Multicycle State Elements

- Replace Instruction and Data memories with a single unified memory
  - More realistic




Copyright © 2007 Elsevier

7-<42>


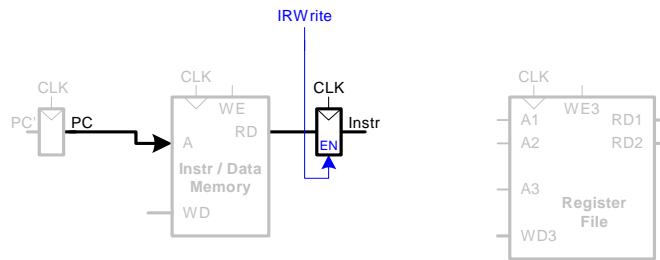
## Multicycle Datapath: instruction fetch

- First consider executing `lw`
- **STEP 1:** Fetch instruction




Copyright © 2007 Elsevier

7-<43>


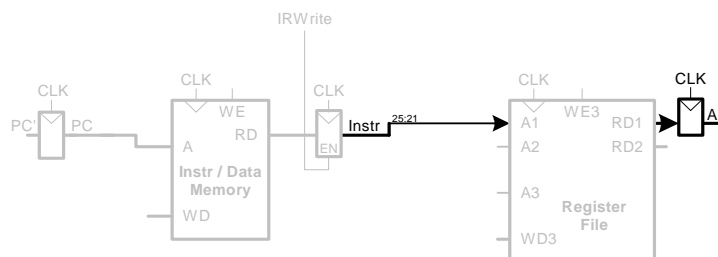
## Multicycle Datapath: `lw` register read




Copyright © 2007 Elsevier

7-<44>



## Multicycle Datapath: $l_w$ immediate

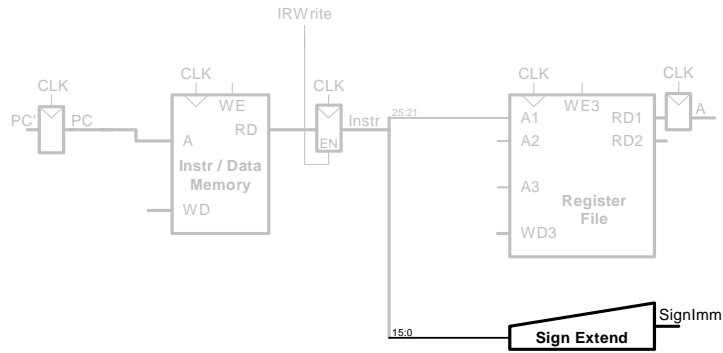


Copyright © 2007 Elsevier

7-<45>



## Multicycle Datapath: $l_w$ address

 


Copyright © 2007 Elsevier

7-<46>


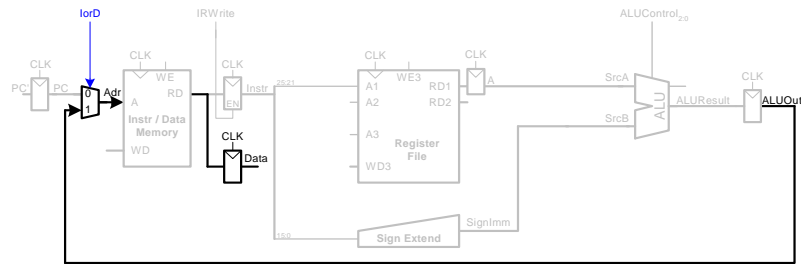
## Multicycle Datapath: $l_w$ memory read




Copyright © 2007 Elsevier

7-<47>


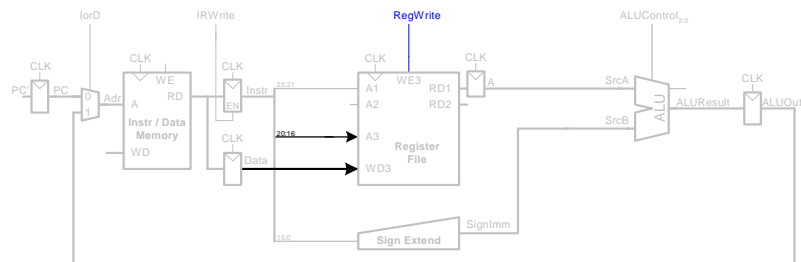
## Multicycle Datapath: $l_w$ write register




Copyright © 2007 Elsevier

7-<48>





## Multicycle Datapath: increment PC

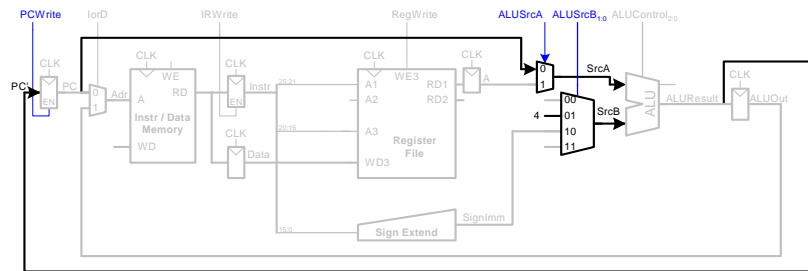


Copyright © 2007 Elsevier

7-<49>



## Multicycle Datapath: SW

- Write data in `rt` to memory

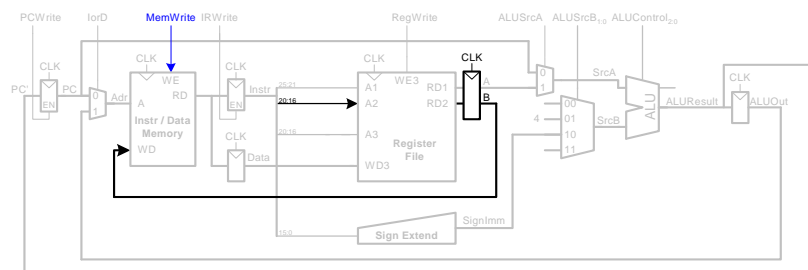


Copyright © 2007 Elsevier

7-<50>


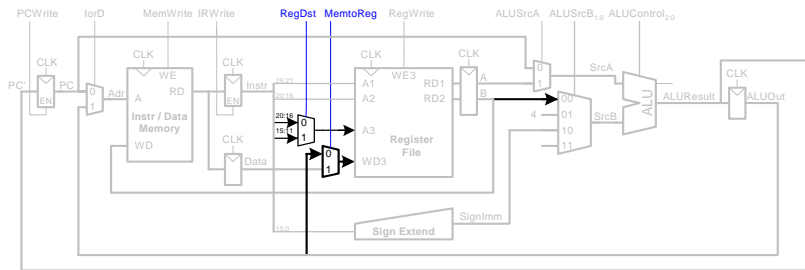
## Multicycle Datapath: R-type Instructions

- Read from *rs* and *rt*
- Write *ALUResult* to register file
- Write to *rd* (instead of *rt*)



Copyright © 2007 Elsevier


7-<51>


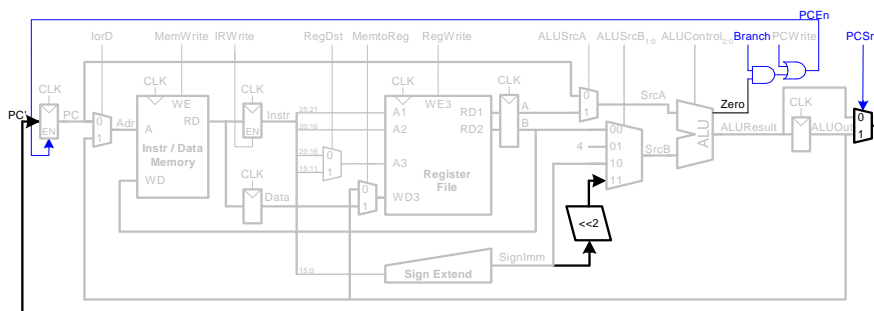
## Multicycle Datapath: beq

- Determine whether values in *rs* and *rt* are equal
- Calculate branch target address:  

$$BTA = (\text{sign-extended immediate} \ll 2) + (PC+4)$$




Copyright © 2007 Elsevier

7-<52>



# Complete Multicycle Processor

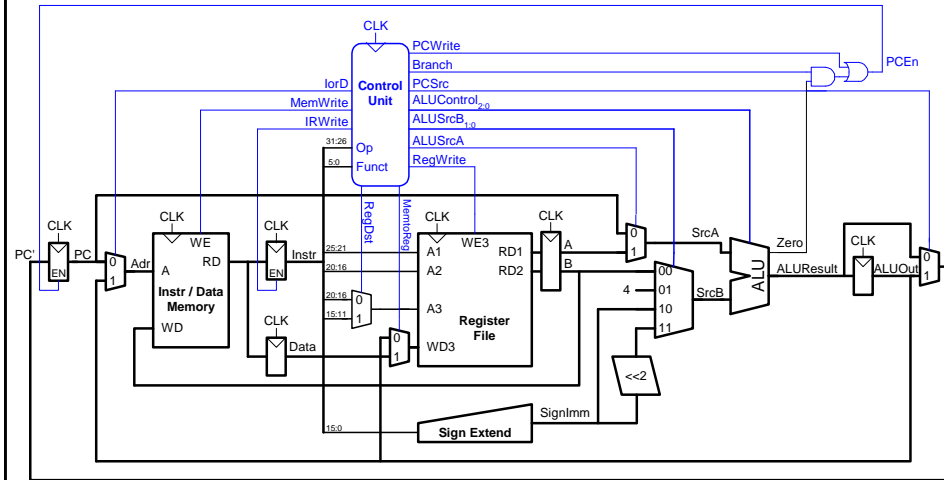


Copyright © 2007 Elsevier

7-<53>



# Control Unit


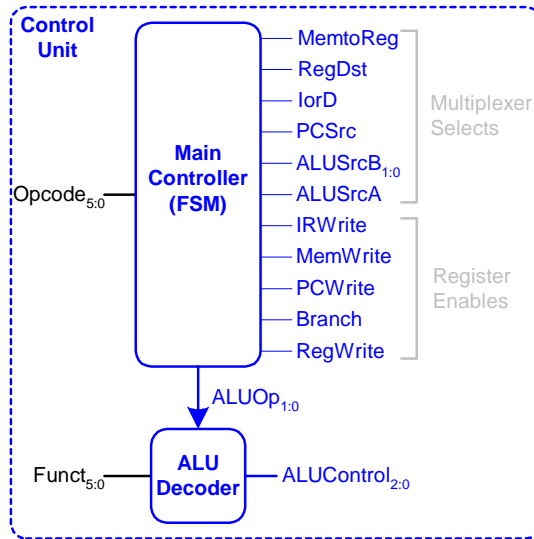


Copyright © 2007 Elsevier

7-<54>



# Main Controller FSM: Fetch

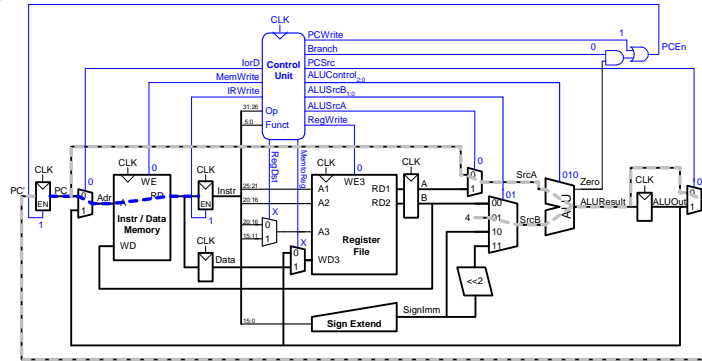
 


Copyright © 2007 Elsevier

7-<55>



# Main Controller FSM: Fetch

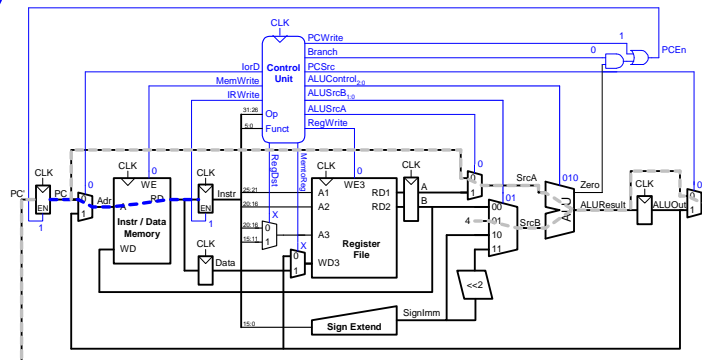 


Copyright © 2007 Elsevier

7-<56>



## Main Controller FSM: Decode

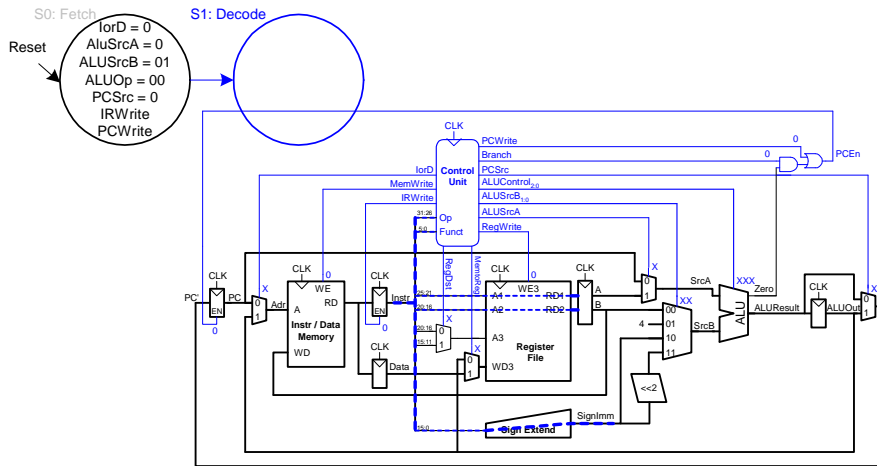


Copyright © 2007 Elsevier

7-<57>


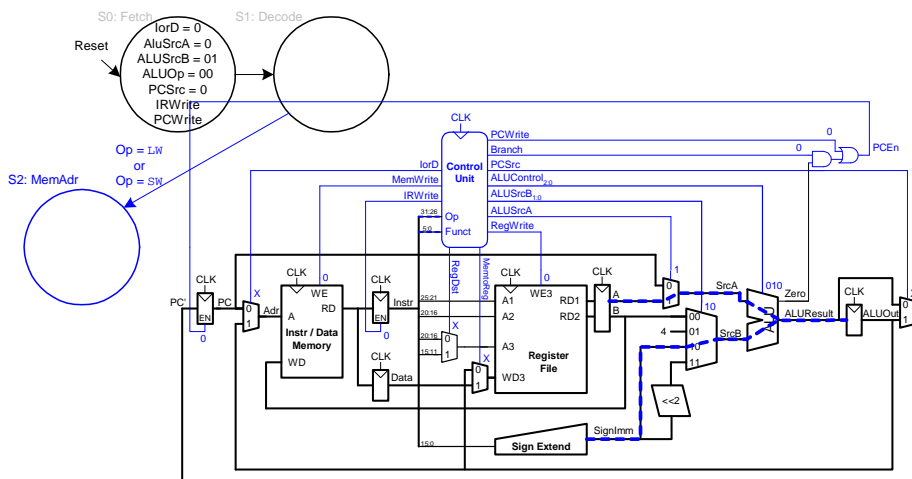
## Main Controller FSM: Address Calculation




Copyright © 2007 Elsevier

7-<58>


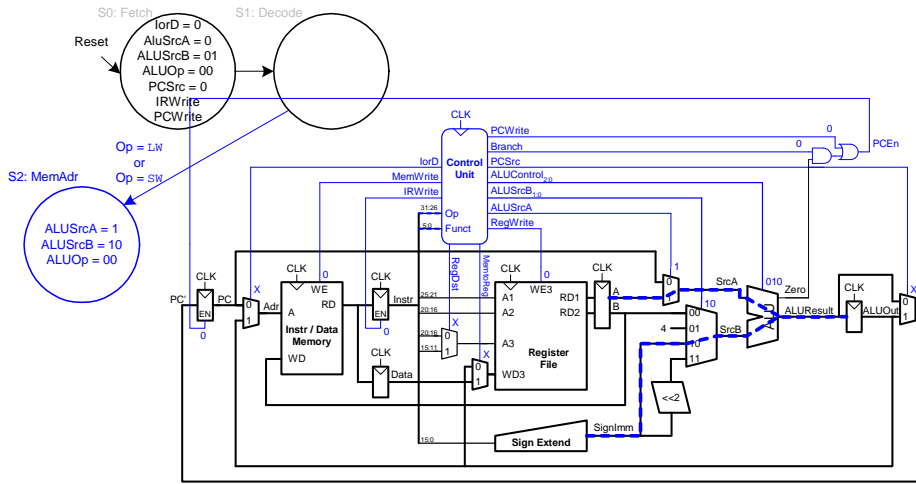
## Main Controller FSM: Address Calculation




Copyright © 2007 Elsevier

7-<59>



## Main Controller FSM: lw

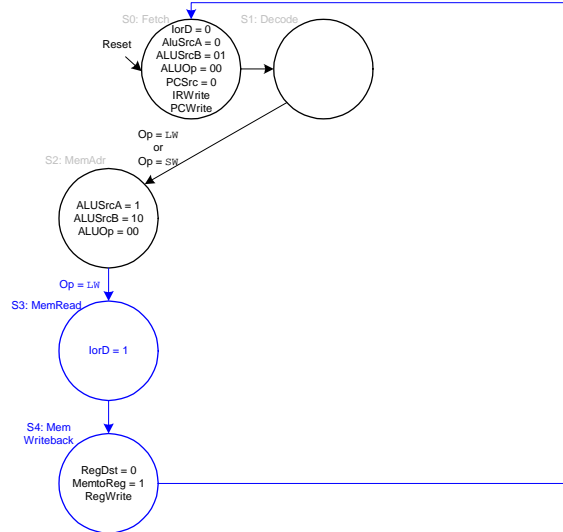


Copyright © 2007 Elsevier

7-<60>




## Main Controller FSM: SW

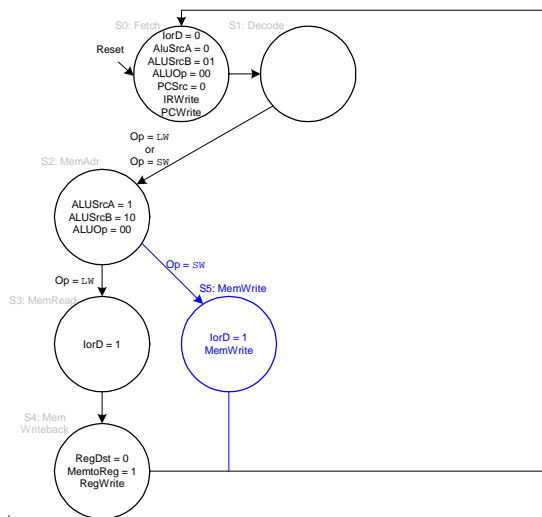

7-<61>




## Main Controller FSM: R-Type

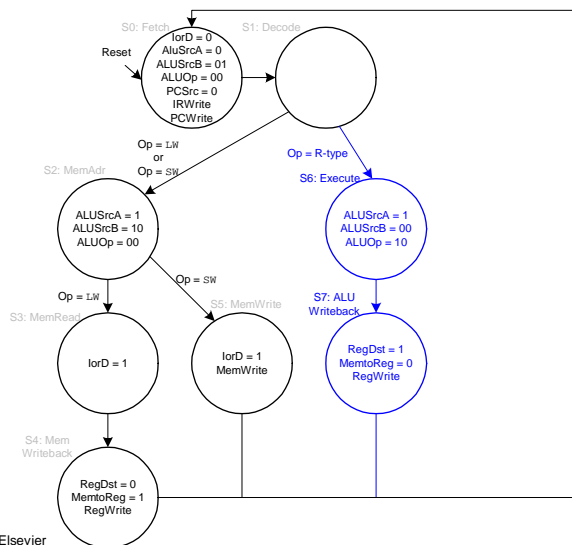

7-<62>



# Main Controller FSM: beq

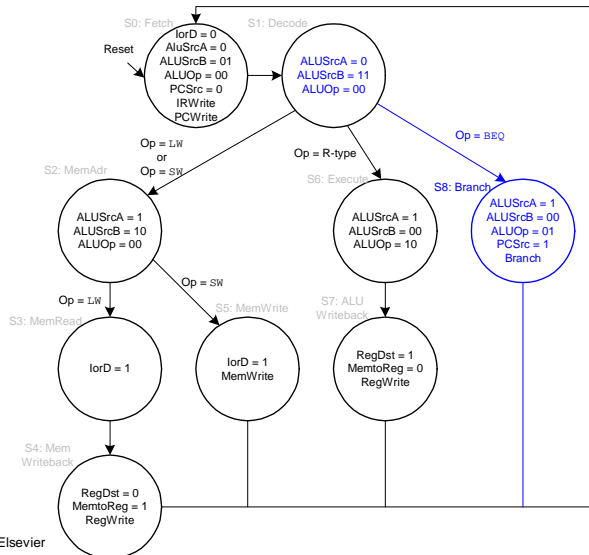


Copyright © 2007 Elsevier

7-<63>



# Complete Multicycle Controller FSM

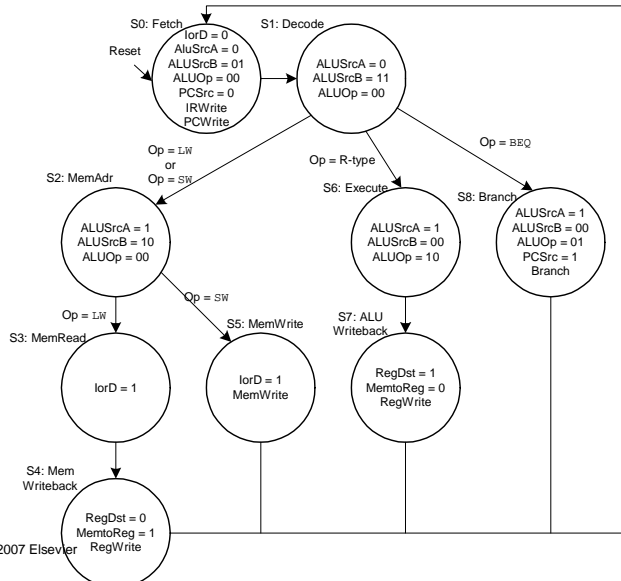


Copyright © 2007 Elsevier

7-<64>






## Main Controller FSM: addi

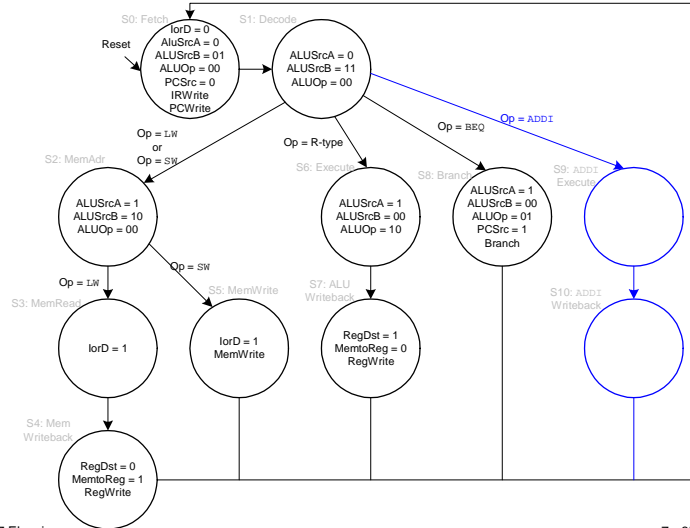

7-<65>




## Main Controller FSM: addi

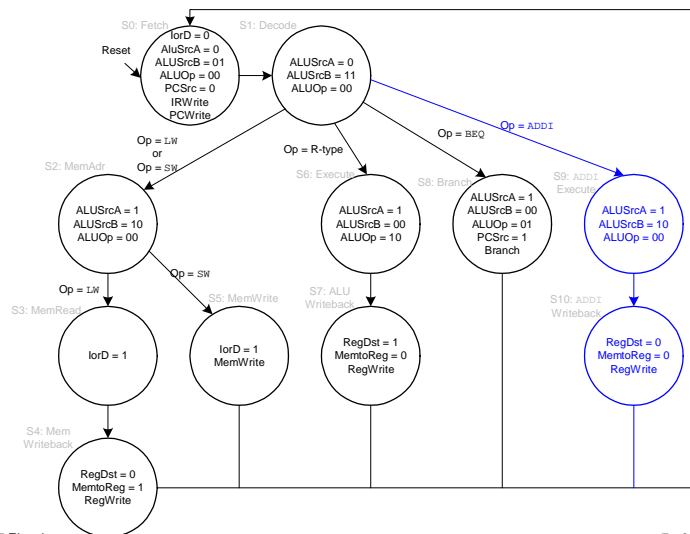

7-<66>



## Extended Functionality: j

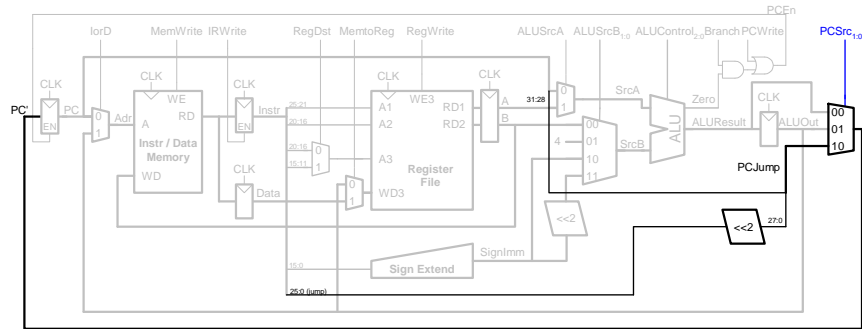


Copyright © 2007 Elsevier

7-67>



## Control FSM: j

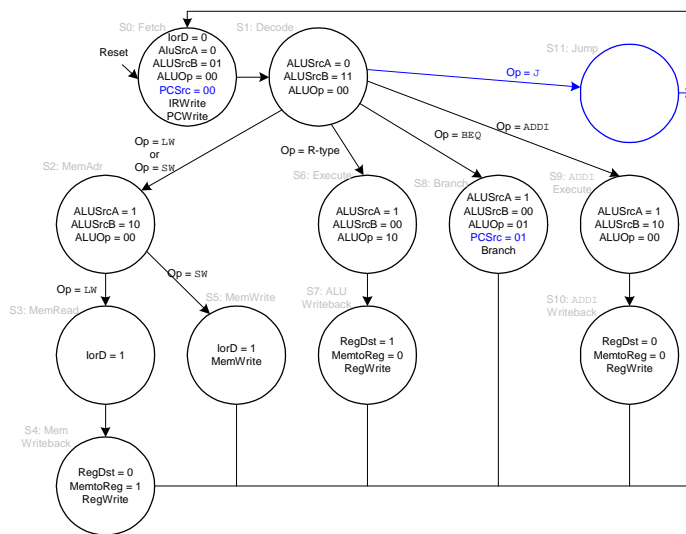


Copyright © 2007 Elsevier

7-68>



## Control FSM: j

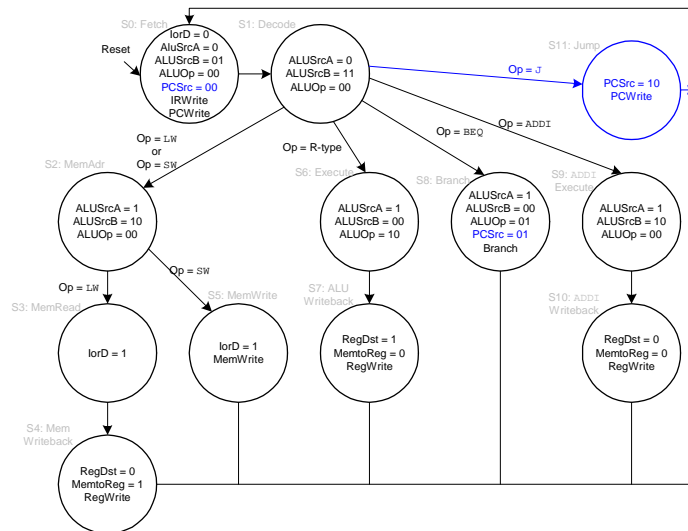

Copyright © 2007 Elsevier

7-<69>



## Multicycle Performance

- Instructions take different number of cycles:
  - 3 cycles: beq, j
  - 4 cycles: R-Type, sw, addi
  - 5 cycles: lw
- CPI is weighted average
- SPECINT2000 benchmark:
  - 25% loads
  - 10% stores
  - 11% branches
  - 2% jumps
  - 52% R-type

$$\text{Average CPI} = (0.11 + 0.2)(3) + (0.52 + 0.10)(4) + (0.25)(5) = 4.12$$

Copyright © 2007 Elsevier


7-<70>



## Multicycle Performance

- Multicycle critical path:

$$T_c =$$

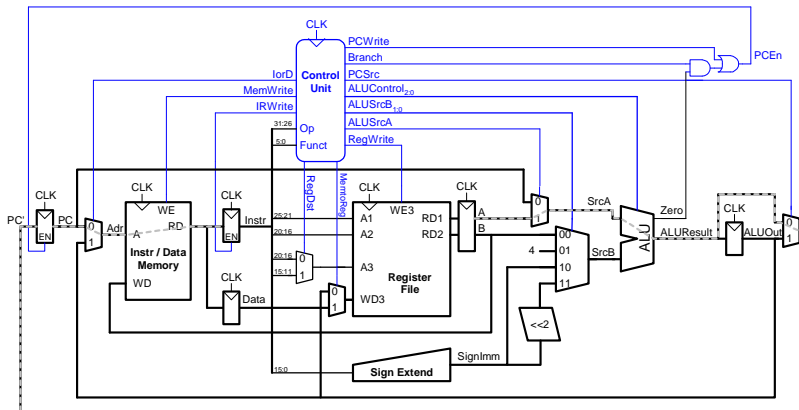

Copyright © 2007 Elsevier


7-<71>


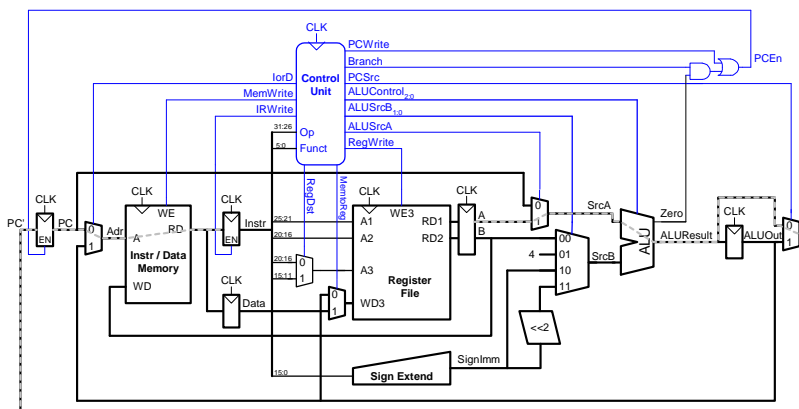
## Multicycle Performance

- Multicycle critical path:

$$T_c = t_{pcq} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$



Copyright © 2007 Elsevier

7-<72>



## Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$T_c =$$

Copyright © 2007 Elsevier

7-<73>



## Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}
 T_c &= t_{pcq\_PC} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup} \\
 &= t_{pcq\_PC} + t_{mux} + t_{mem} + t_{setup} \\
 &= [30 + 25 + 250 + 20] \text{ ps} \\
 &= 325 \text{ ps}
 \end{aligned}$$

Copyright © 2007 Elsevier

7-<74>



## Multicycle Performance Example

- For a program with 100 billion instructions executing on a multicycle MIPS processor
  - CPI = 4.12
  - $T_c = 325$  ps

Execution Time =

Copyright © 2007 Elsevier

7-<75>



## Multicycle Performance Example

- For a program with 100 billion instructions executing on a multicycle MIPS processor
  - CPI = 4.12
  - $T_c = 325$  ps

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(325 \times 10^{-12}) \\ &= 133.9 \text{ seconds}\end{aligned}$$

- This is **slower** than the single-cycle processor (92.5 seconds). Why?

Copyright © 2007 Elsevier

7-<76>



## Multicycle Performance Example

- For a program with 100 billion instructions executing on a multicycle MIPS processor
  - CPI = 4.12
  - $T_c = 325$  ps

$$\begin{aligned} \text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(325 \times 10^{-12}) \\ &= 133.9 \text{ seconds} \end{aligned}$$


- This is **slower** than the single-cycle processor (92.5 seconds). Why?
  - Not all steps the same length
  - Sequencing overhead for each step ( $t_{pcq} + t_{\text{setup}} = 50$  ps)

Copyright © 2007 Elsevier

7-<77>



## Review: Single-Cycle MIPS Processor

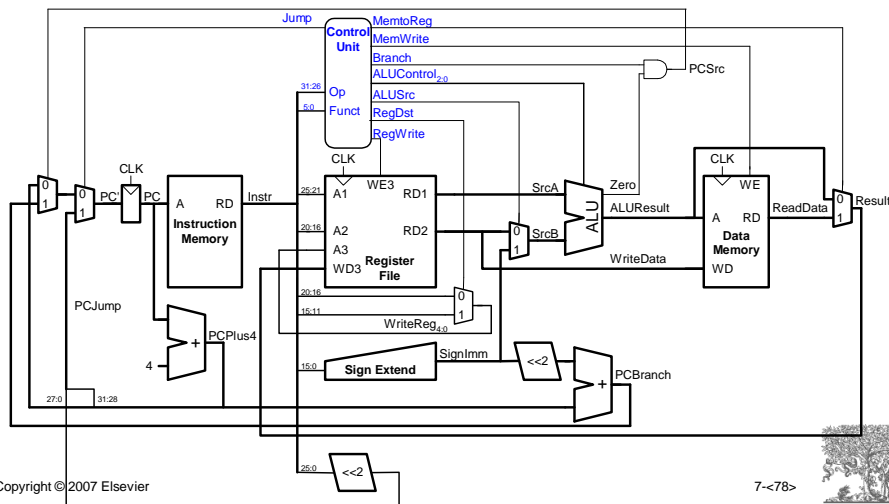


Copyright © 2007 Elsevier

7-<78>



## Review: Multicycle MIPS Processor

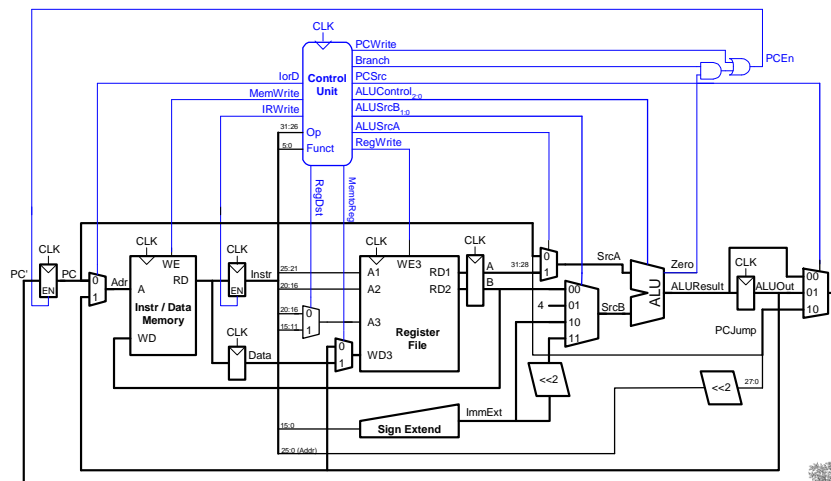

Copyright © 2007 Elsevier

7-<79>



## Pipelined MIPS Processor

- Temporal parallelism
- Divide single-cycle processor into 5 stages:
  - Fetch
  - Decode
  - Execute
  - Memory
  - Writeback
- Add pipeline registers between stages

Copyright © 2007 Elsevier


7-<80>






# Single-Cycle vs. Pipelined Performance

## Single-Cycle

 

## Pipelined

 


Copyright © 2007 Elsevier

7-<81>



# Pipelining Abstraction


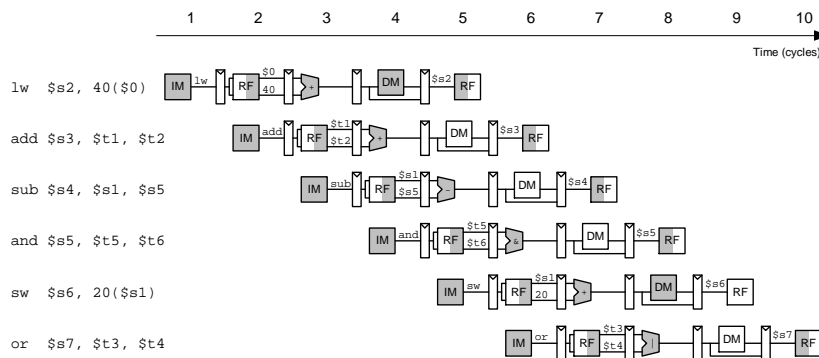


Copyright © 2007 Elsevier

7-<82>



## Single-Cycle and Pipelined Datapath

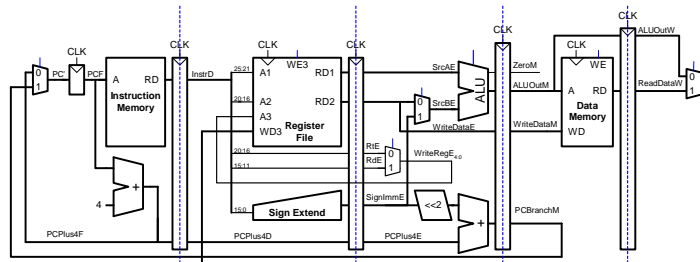 

Copyright © 2007 Elsevier

Fetch

Decode

Execute

Memory


Writeback

7-<83>


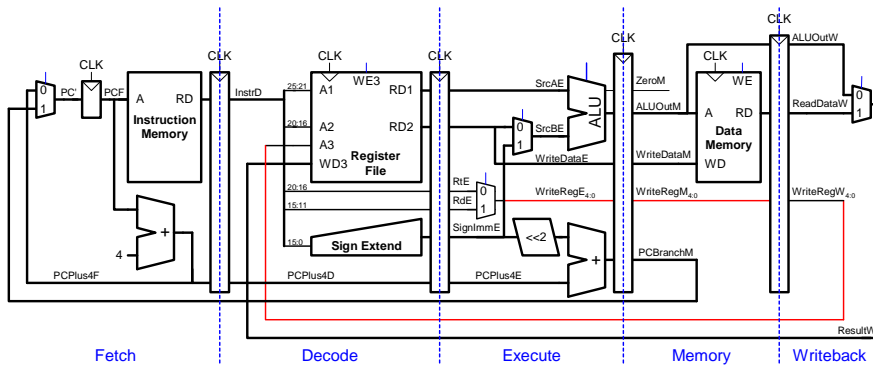
## Corrected Pipelined Datapath

- WriteReg must arrive at the same time as Result




Copyright © 2007 Elsevier

7-<84>



## Pipelined Control

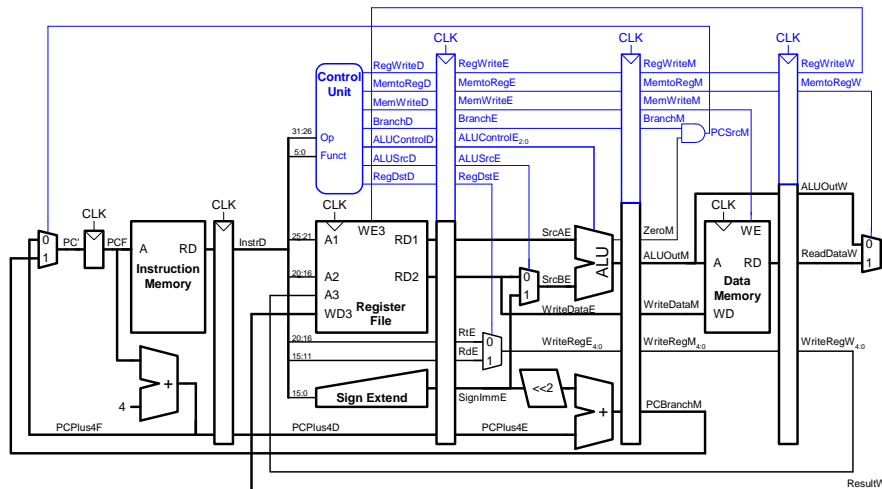

Same control unit as single-cycle processor

Control delayed to proper pipeline stage

Copyright © 2007 Elsevier

7-85>



## Pipeline Hazard


- Occurs when an instruction depends on results from previous instruction that hasn't completed.
- Types of hazards:
  - **Data hazard:** register value not written back to register file yet
  - **Control hazard:** next instruction not decided yet (caused by branches)

Copyright © 2007 Elsevier

7-86>



## Data Hazard

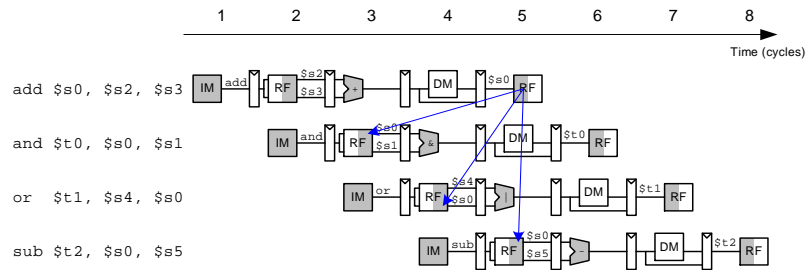

Copyright © 2007 Elsevier

7-<87>



## Handling Data Hazards

- Insert nops in code at compile time
- Rearrange code at compile time
- Forward data at run time
- Stall the processor at run time


Copyright © 2007 Elsevier

7-<88>


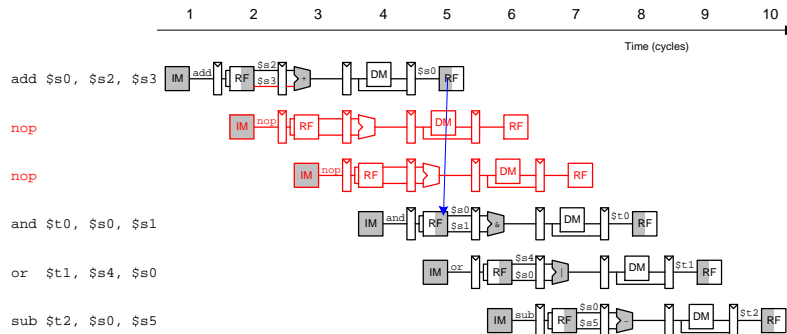
## Compile-Time Hazard Elimination

- Insert enough nops for result to be ready
- Or move independent useful instructions forward




Copyright © 2007 Elsevier

7-89



## Data Forwarding

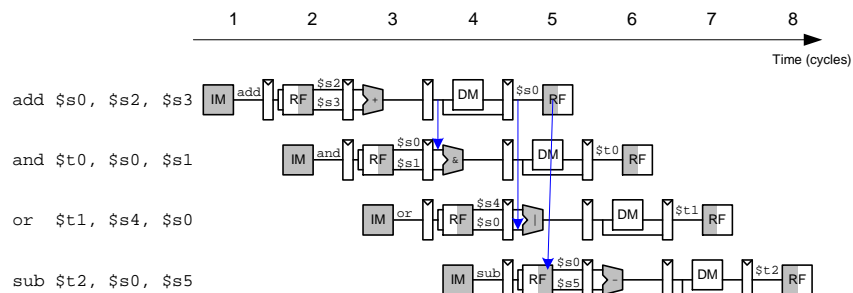


Copyright © 2007 Elsevier

7-90



## Data Forwarding

 

Copyright © 2007 Elsevier

7-<91>



## Data Forwarding

- Forward to Execute stage from either:
  - Memory stage or
  - Writeback stage
- Forwarding logic for *ForwardAE*:
 

```


if      ((rsE != 0) AND (rsE == WriteRegM) AND RegWriteM)
then    ForwardAE = 10
else if ((rsE != 0) AND (rsE == WriteRegW) AND RegWriteW)
then    ForwardAE = 01
else    ForwardAE = 00
            
```
- Forwarding logic for *ForwardBE* same, but replace *rsE* with *rtE*

Copyright © 2007 Elsevier

7-<92>



# Stalling

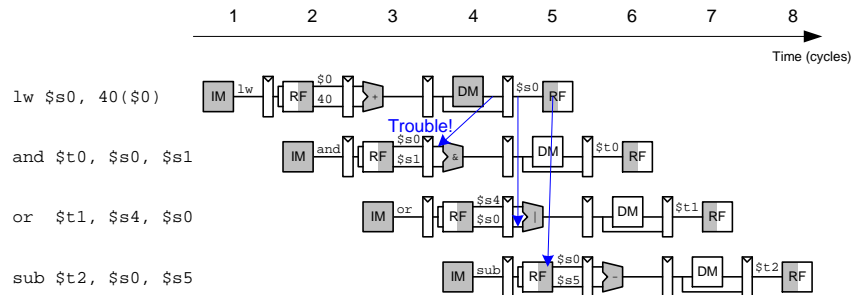


Copyright © 2007 Elsevier

7-<93>



# Stalling

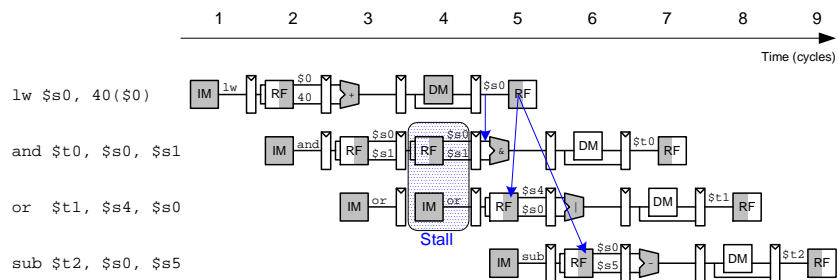


Copyright © 2007 Elsevier

7-<94>



## Stalling Hardware

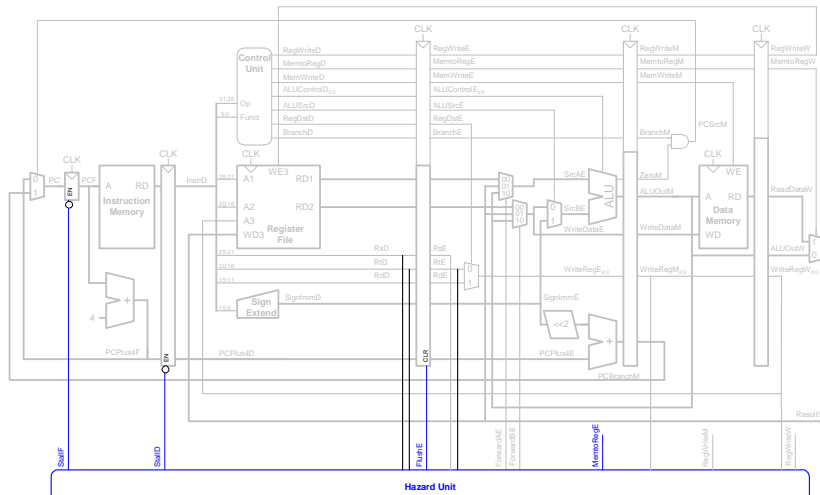

Copyright © 2007 Elsevier

7-<95>



## Stalling Hardware

- Stalling logic:

$$lwstall = ((rsD == rtE) \text{ OR } (rtD == rtE)) \text{ AND MemtoRegE}$$

$$StallF = StallD = FlushE = lwstall$$

Copyright © 2007 Elsevier

7-<96>





## Control Hazards


- `beq`:
  - branch is not determined until the fourth stage of the pipeline
  - Instructions after the branch are fetched before branch occurs
  - These instructions must be flushed if the branch happens
- Branch misprediction penalty
  - number of instruction flushed when branch is taken
  - May be reduced by determining branch earlier

Copyright © 2007 Elsevier

7--<97>



## Control Hazards: Original Pipeline

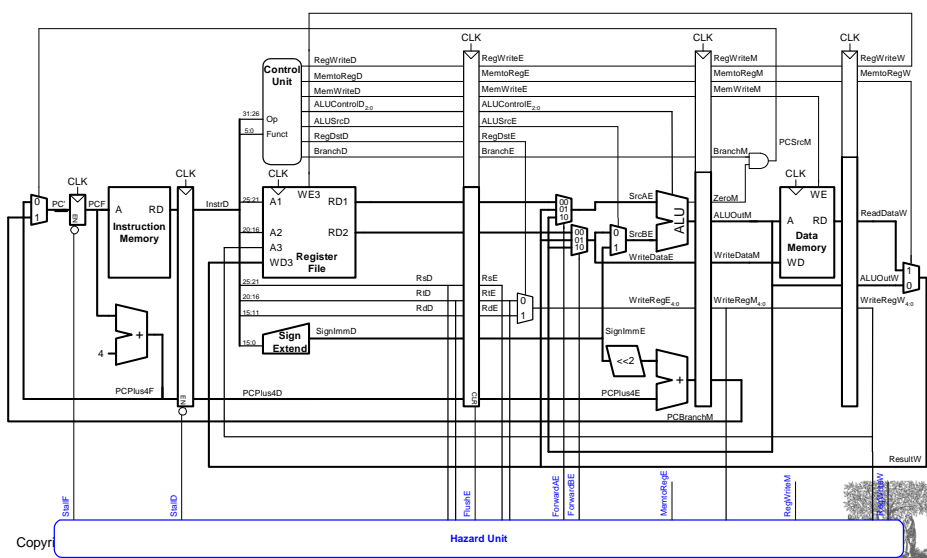


Copyr

Hazard Unit



# Control Hazards

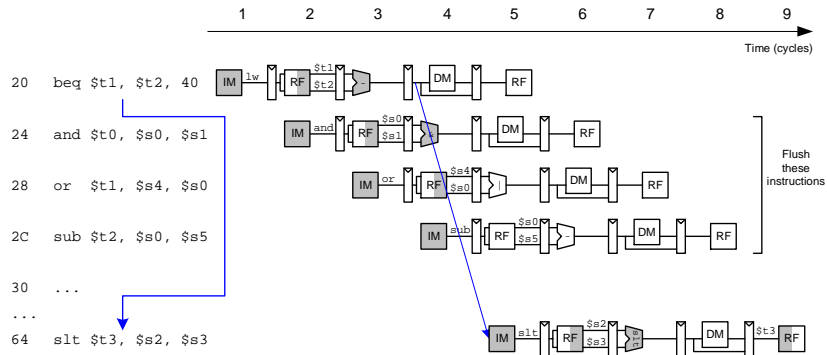


Copyright © 2007 Elsevier

7-<99>


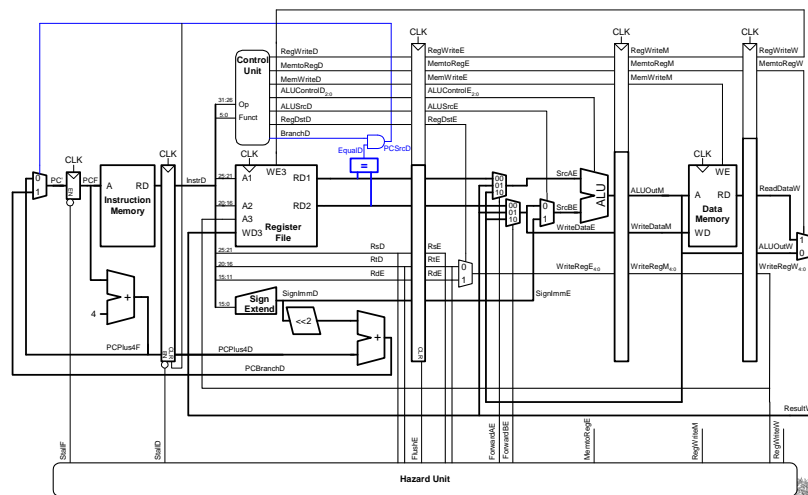
# Control Hazards: Early Branch Resolution




Copyright © 2007 Elsevier

Introduced another data hazard in Decode stage

7-<100>


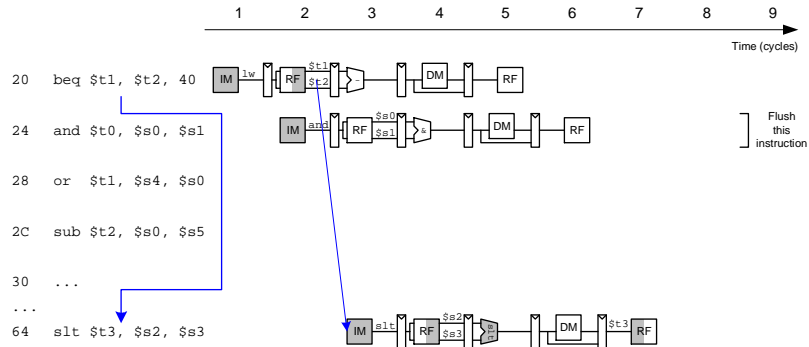
## Control Hazards with Early Branch Resolution




Copyright © 2007 Elsevier

7-101>



## Handling Data and Control Hazards

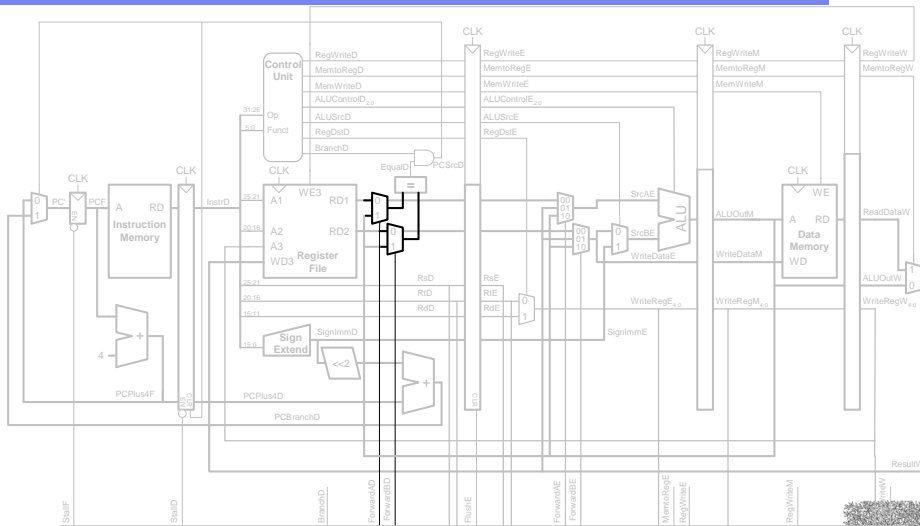

Copyright © 2007 Elsevier

7-101>



## Control Forwarding and Stalling Hardware

- Forwarding logic:

*ForwardAD = (rsD != 0) AND (rsD == WriteRegM) AND RegWriteM*

*ForwardBD = (rtD != 0) AND (rtD == WriteRegM) AND RegWriteM*

- Stalling logic:

*branchstall = BranchD AND RegWriteE AND  
(WriteRegE == rsD OR WriteRegE == rtD)*

OR

*BranchD AND MemtoRegM AND  
(WriteRegM == rsD OR WriteRegM == rtD)*

*StallF = StallD = FlushE = lwstall OR branchstall*

Copyright © 2007 Elsevier

7-<103>



## Branch Prediction

- Guess whether branch will be taken
  - Backward branches are usually taken (loops)
  - Perhaps consider history of whether branch was previously taken to improve the guess
- Good prediction reduces the fraction of branches requiring a flush

Copyright © 2007 Elsevier

7-<104>



## Pipelined Performance Example

- Ideally CPI = 1
- But need to handle stalling (caused by loads and branches)
- SPECINT2000 benchmark:
  - 25% loads
  - 10% stores
  - 11% branches
  - 2% jumps
  - 52% R-type
- Suppose:
  - 40% of loads used by next instruction
  - 25% of branches mispredicted
- **What is the average CPI?**

Copyright © 2007 Elsevier

7-<105>



## Pipelined Performance Example

- SPECINT2000 benchmark:
  - 25% loads
  - 10% stores
  - 11% branches
  - 2% jumps
  - 52% R-type
- Suppose:
  - 40% of loads used by next instruction
  - 25% of branches mispredicted
  - All jumps flush next instruction
- **What is the average CPI?**
  - Load/Branch CPI = 1 when no stalling, 2 when stalling. Thus,
  - $CPI_{lw} = 1(0.6) + 2(0.4) = 1.4$
  - $CPI_{beq} = 1(0.75) + 2(0.25) = 1.25$
  - Thus,

$$\text{Average CPI} = (0.25)(1.4) + (0.1)(1) + (0.11)(1.25) + (0.02)(2) + (0.52)(1) = 1.15$$

Copyright © 2007 Elsevier

7-<106>



## Pipelined Performance

- Pipelined processor critical path:

$$T_c = \max \{$$

$$t_{pcq} + t_{mem} + t_{setup}$$

$$2(t_{RFread} + t_{mux} + t_{eq} + t_{AND} + t_{mux} + t_{setup})$$

$$t_{pcq} + t_{mux} + t_{mux} + t_{ALU} + t_{setup}$$

$$t_{pcq} + t_{memwrite} + t_{setup}$$

$$2(t_{pcq} + t_{mux} + t_{RFwrite}) \}$$

Copyright © 2007 Elsevier

7-<107>



## Pipelined Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	30
Register setup	$t_{setup}$	20
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	200
Memory read	$t_{mem}$	250
Register file read	$t_{RFread}$	150
Register file setup	$t_{RFsetup}$	20
Equality comparator	$t_{eq}$	40
AND gate	$t_{AND}$	15
Memory write	$T_{memwrite}$	220
Register file write	$t_{RFwrite}$	100 ps

$$T_c = 2(t_{RFread} + t_{mux} + t_{eq} + t_{AND} + t_{mux} + t_{setup})$$

$$= 2[150 + 25 + 40 + 15 + 25 + 20] \text{ ps} = 550 \text{ ps}$$

Copyright © 2007 Elsevier

7-<108>



## Pipelined Performance Example

- For a program with 100 billion instructions executing on a pipelined MIPS processor,
- $CPI = 1.15$
- $T_c = 550$  ps

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times CPI \times T_c \\ &= (100 \times 10^9)(1.15)(550 \times 10^{-12}) \\ &= 63 \text{ seconds}\end{aligned}$$

Processor	Execution Time (seconds)	Speedup (single-cycle is baseline)
Single-cycle	95	1
Multicycle	133	0.71
Pipelined	63	1.51

Copyright © 2007 Elsevier

7-<109>



## Review: Exceptions

- Unscheduled procedure call to the *exception handler*
- Caused by:
  - Hardware, also called an *interrupt*, e.g. keyboard
  - Software, also called *traps*, e.g. undefined instruction
- When exception occurs, the processor:
  - Records the cause of the exception (Cause register)
  - Jumps to the exception handler at instruction address 0x80000180
  - Returns to program (EPC register)

Copyright © 2007 Elsevier

7-<110>





## Example Exception

sequential circuits.]

Can we design a spiff

Figure 2.11 shows a  
inputs, A and B, and on  
box indicates that it is  
this case, the function is

 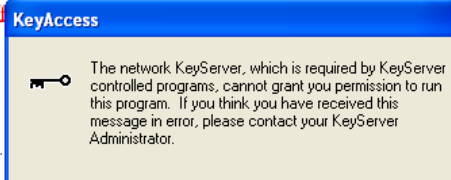

words, we say the output Y is a function of the two inputs A and B where  
the function performed is A OR B.]

The *implementation* of the combinational circuit is independent of its  
functionality. Figure 2.1 and Figure 2.2 show two possible implementations.

Copyright © 2007 Elsevier

7-<111>



## Exception Registers

- Not part of the register file.
  - Cause
    - Records the cause of the exception
    - Coprocessor 0 register 13
  - EPC (Exception PC)
    - Records the PC where the exception occurred
    - Coprocessor 0 register 14
- Move from Coprocessor 0
  - mfc0 \$t0, Cause
  - Moves the contents of Cause into \$t0

**mfc0**

010000	00000	\$t0 (8)	Cause (13)	00000000000
31:26	25:21	20:16	15:11	10:0

Copyright © 2007 Elsevier

7-<112>





## Exception Causes

Exception	Cause
Hardware Interrupt	0x00000000
System Call	0x00000020
Breakpoint / Divide by 0	0x00000024
Undefined Instruction	0x00000028
Arithmetic Overflow	0x00000030


We extend the multicycle MIPS processor to handle the last two types of exceptions.

Copyright © 2007 Elsevier

7-<113>



## Exception Hardware: EPC & Cause

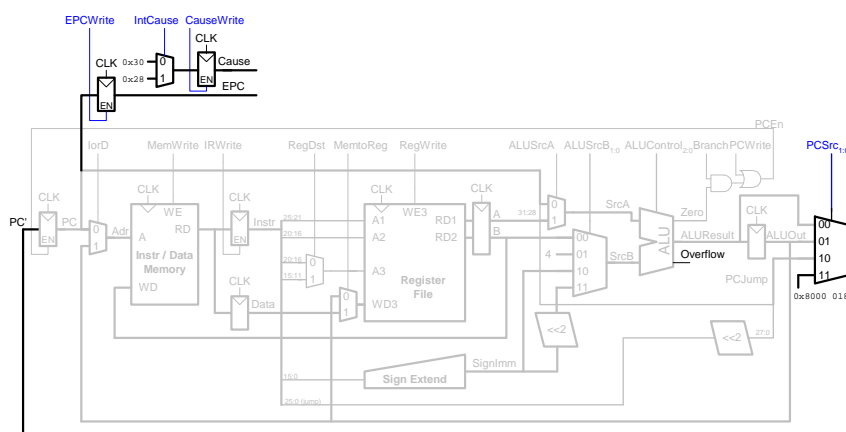


Copyright © 2007 Elsevier

7-<114>



# Exception Hardware: mfc0

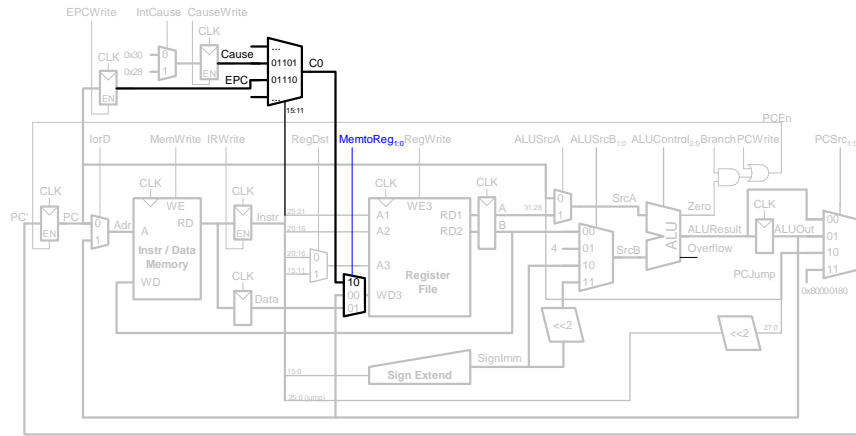


Copyright © 2007 Elsevier

7-<115>



# Control FSM with Exceptions

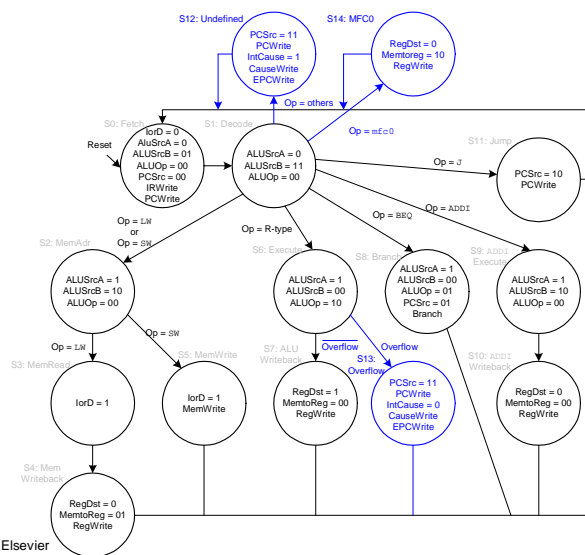

Copyright © 2007 Elsevier

7-<116>



## Advanced MicroArchitecture

- Deep Pipelining
- Branch Prediction
- Superscalar Processors
- Out of Order Processors
- Register Renaming
- SIMD
- Multithreading
- Multiprocessors

Copyright © 2007 Elsevier

7-<117>



## Deep Pipelining

- 10-20 stages typical
- Number of stages limited by:
  - Pipeline hazards
  - Sequencing overhead
  - Power
  - Cost

Copyright © 2007 Elsevier

7-<118>



## Branch Prediction

- Ideal pipelined processor:  $CPI = 1$
- Branch misprediction increases CPI
- Static branch prediction:
  - Check direction of branch (forward or backward)
  - If backward, predict taken
  - Otherwise, predict not taken
- Dynamic branch prediction:
  - Keep history of last (several hundred) branches in a *branch target buffer* which holds:
    - Branch destination
    - Whether branch was taken

Copyright © 2007 Elsevier

7-<119>



## Branch Prediction Example

```
add  $s1, $0, $0      # sum = 0
add  $s0, $0, $0      # i  = 0
addi $t0, $0, 10      # $t0 = 10
for:
    beq  $t0, $t0, done # if i == 10, branch
    add  $s1, $s1, $s0  # sum = sum + i
    addi $s0, $s0, 1    # increment i
    j    for
done:
```

Copyright © 2007 Elsevier

7-<120>



## 1-Bit Branch Predictor

- Remembers whether branch was taken the last time and does the same thing
- Mispredicts first and last branch of loop


Copyright © 2007 Elsevier

7-<121>



## 2-Bit Branch Predictor

- Only mispredicts last branch of loop

 


Copyright © 2007 Elsevier

7-<122>


 
## Superscalar

- Multiple copies of datapath execute multiple instructions at once
- Dependencies make it tricky to issue multiple instructions at once



Copyright © 2007 Elsevier

7-<123>




## Superscalar Example

```

lw $t0, 40($s0)
add $t1, $t0, $s1
sub $t0, $s2, $s3
and $t2, $s4, $t0
or $t3, $s5, $s6
sw $s7, 80($t3)
    
```

Ideal IPC: 2

Actual IPC: 2

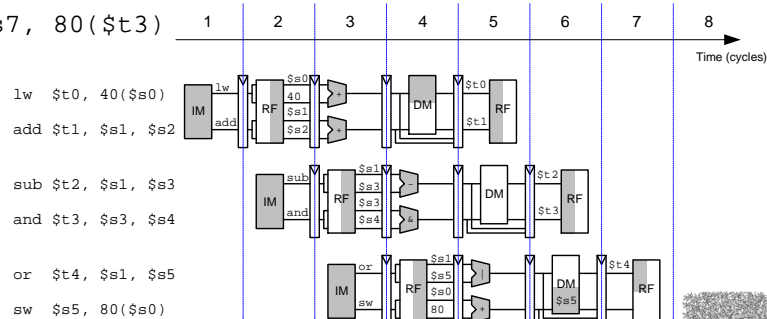

Copyright © 2007 Elsevier


7-<124>



## Superscalar Example with Dependencies

```
lw $t0, 40($s0)
add $t1, $t0, $s1
sub $t0, $s2, $s3
and $t2, $s4, $t0
or $t3, $s5, $s6
sw $s7, 80($t3)
```

Ideal IPC: 2  
Actual IPC:  $6/5 = 1.17$

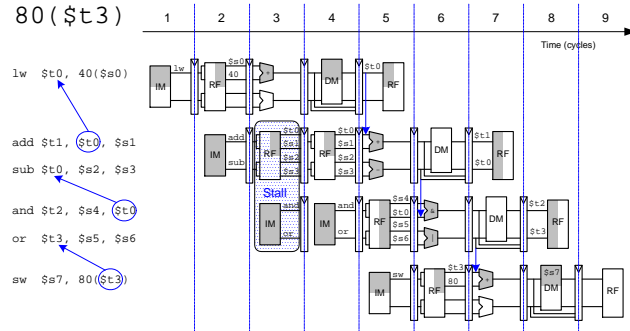

Copyright © 2007 Elsevier

7-<125>



## Out of Order Processor

- Looks ahead across multiple instructions to issue as many as possible at once
- Issues instructions out of order as long as no dependencies
- Dependencies:
  - **RAW** (read after write): one instruction writes, and later instruction reads a register
  - **WAR** (write after read): one instruction reads, and a later instruction writes a register (also called an *antidependence*)
  - **WAW** (write after write): one instruction writes, and a later instruction writes a register (also called an *output dependence*)

Copyright © 2007 Elsevier

7-<126>



## Out of Order Processor

- **Instruction level parallelism:** the number of instruction that can be issued simultaneously (in practice average < 3)
- **Scoreboard:** table that keeps track of:
  - Instructions waiting to issue
  - Available functional units
  - Dependencies

Copyright © 2007 Elsevier

7-<127>




## Out of Order Processor Example

```

lw $t0, 40($s0)
add $t1, $t0, $s1
sub $t0, $s2, $s3
and $t2, $s4, $t0
or $t3, $s5, $s6
sw $s7, 80($t3)
    
```

Ideal IPC: 2  
Actual IPC: 6/4 = 1.5

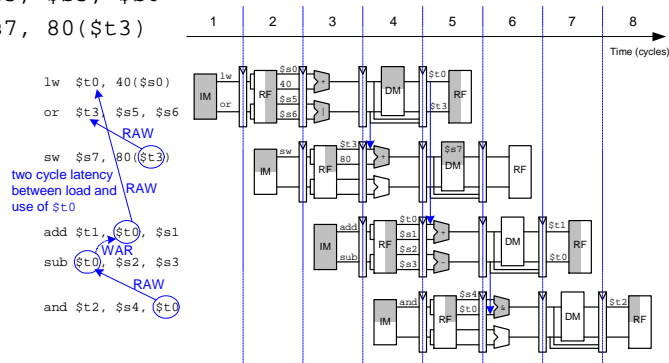

Copyright © 2007 Elsevier

7-<128>






## Register Renaming

```
lw $t0, 40($s0)
add $t1, $t0, $s1
sub $t0, $s2, $s3
and $t2, $s4, $t0
or $t3, $s5, $s6
sw $s7, 80($t3)
```

Ideal IPC: 2  
Actual IPC:  $6/3 = 2$

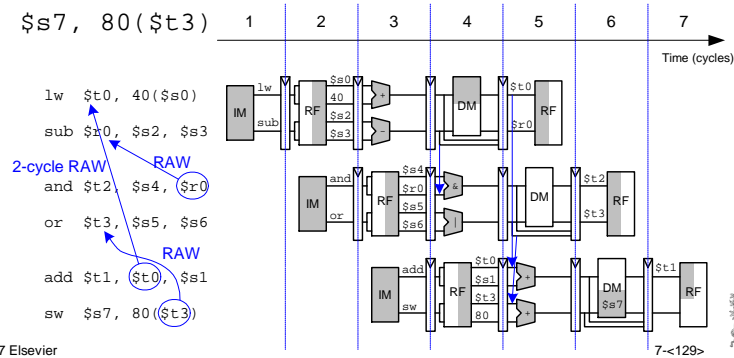


Copyright © 2007 Elsevier



## SIMD

- Single Instruction Multiple Data (SIMD)
  - Single instruction acts on multiple pieces of data at once
  - Common application: graphics
  - Perform short arithmetic operations (also called *packed arithmetic*)
- For example, add four 8-bit elements
- Must modify ALU to eliminate carries between 8-bit values

```
padd8 $s2, $s0, $s1
```

 

Copyright © 2007 Elsevier

7-<130>



## Advanced Architecture Techniques

- Multithreading
  - Wordprocessor: thread for typing, spell checking, printing
- Multiprocessors
  - Multiple processors (cores) on a single chip

Copyright © 2007 Elsevier

7-<131>



## Multithreading: First Some Definitions

- **Process:** program running on a computer
- Multiple processes can run at once: e.g., surfing Web, playing music, writing a paper
- **Thread:** part of a program
- Each process has multiple threads: e.g., a word processor may have threads for typing, spell checking, printing
- In a conventional processor:
  - One thread runs at once
  - When one thread stalls (for example, waiting for memory):
    - Architectural state of that thread is stored
    - Architectural state of waiting thread is loaded into processor and it runs
    - Called **context switching**
  - But appears to user like all threads running simultaneously

Copyright © 2007 Elsevier

7-<132>



## Threads in Conventional Processor

- One thread runs at once
- When one thread stalls (for example, waiting for memory):
  - Architectural state of that thread is stored
  - Architectural state of waiting thread is loaded into processor and it runs
  - Called **context switching**
- Appears to user like all threads running simultaneously

Copyright © 2007 Elsevier

7-<133>



## Multithreading

- Multiple copies of architectural state
- Multiple threads **active** at once:
  - When one thread stalls, another runs immediately (no need to store or restore architectural state)
  - If one thread can't keep all execution units busy, another thread can use them
- Does not increase instruction-level parallelism (ILP) of single thread, but does increase throughput

Copyright © 2007 Elsevier

7-<134>



## Multiprocessors

- Multiple processors (cores) with a method of communication between them
- Types of multiprocessing:
  - **Symmetric multiprocessing (SMT)**: multiple cores with a shared memory
  - **Asymmetric multiprocessing**: separate cores for different tasks (for example, DSP and CPU in cell phone)
  - **Clusters**: each core has its own memory system

Copyright © 2007 Elsevier

7-<135>



## Other Resources

- Patterson & Hennessy's: *Computer Architecture: A Quantitative Approach*
- Conferences:
  - [www.cs.wisc.edu/~arch/www/](http://www.cs.wisc.edu/~arch/www/)
  - ISCA (International Symposium on Computer Architecture)
  - HPCA (International Symposium on High Performance Computer Architecture)

Copyright © 2007 Elsevier

7-<136>

